



Department of Electronics and Electrical engineering

Submitted to:

Mohammed Mosaddique Nawaz Hussain

Associate Professor

EEE department

Submitted by:

PramodVipparthi(244102112)

BhupendraKumarThakur(244102101)

M.tech

Power engineering

➤ **Simulation of buck converter in Altium :**

Circuit Diagram:

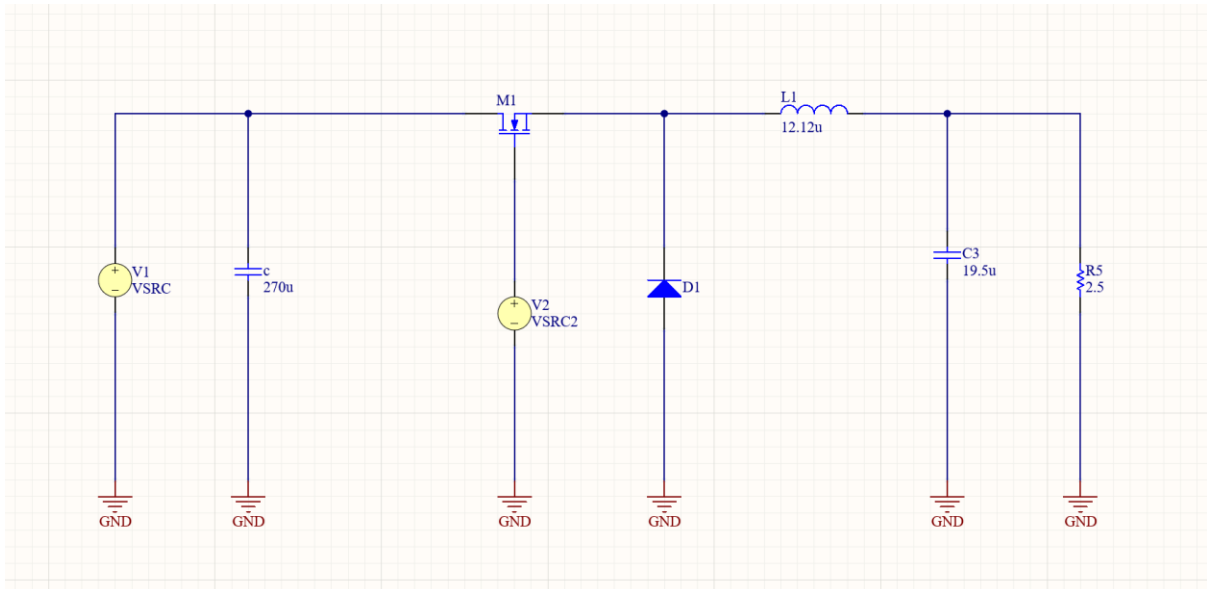



Fig:Schematic of buck converter.

SCHEMATIC VERIFICATION BEFORE GETTING SIMULATION RESULTS:

STEPS AND PROCEDURE:

Place all the components as per the data sheet provided with values. After schematic representation, we have to do **Verification check** ie.,


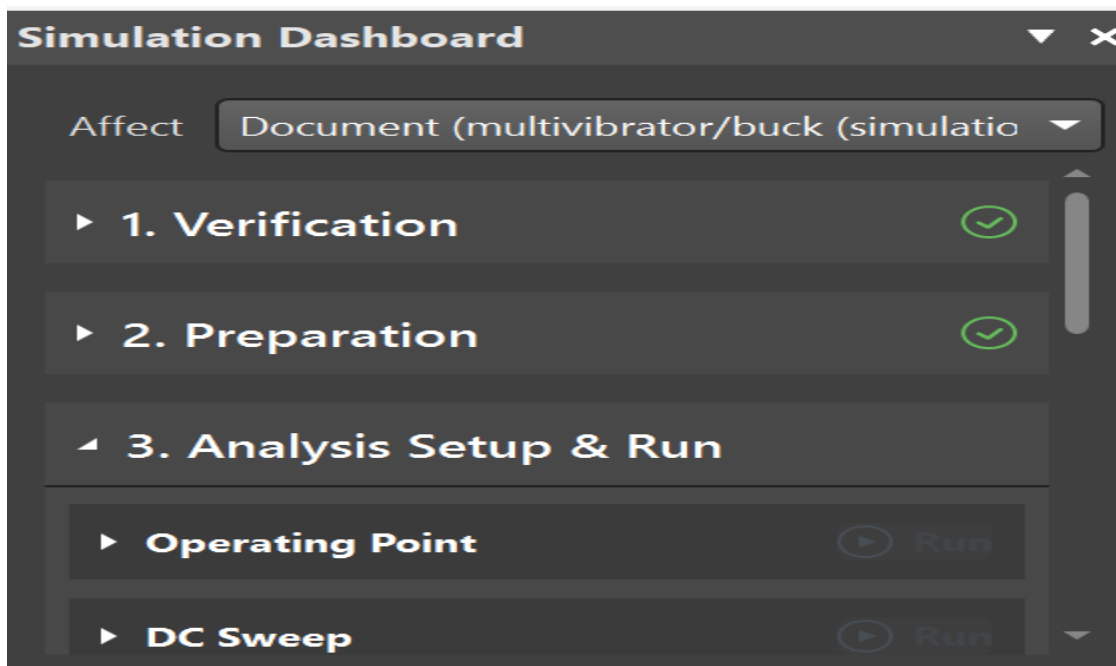
Open Simulate>Simulation_Dashboard>Start Verification. Next



After successful verification of Electrical Rule check and Simulation model Next

Go to **Analysis Setup & Run> Transient > Set Time period 1msec to 100nsec > run**

Results:

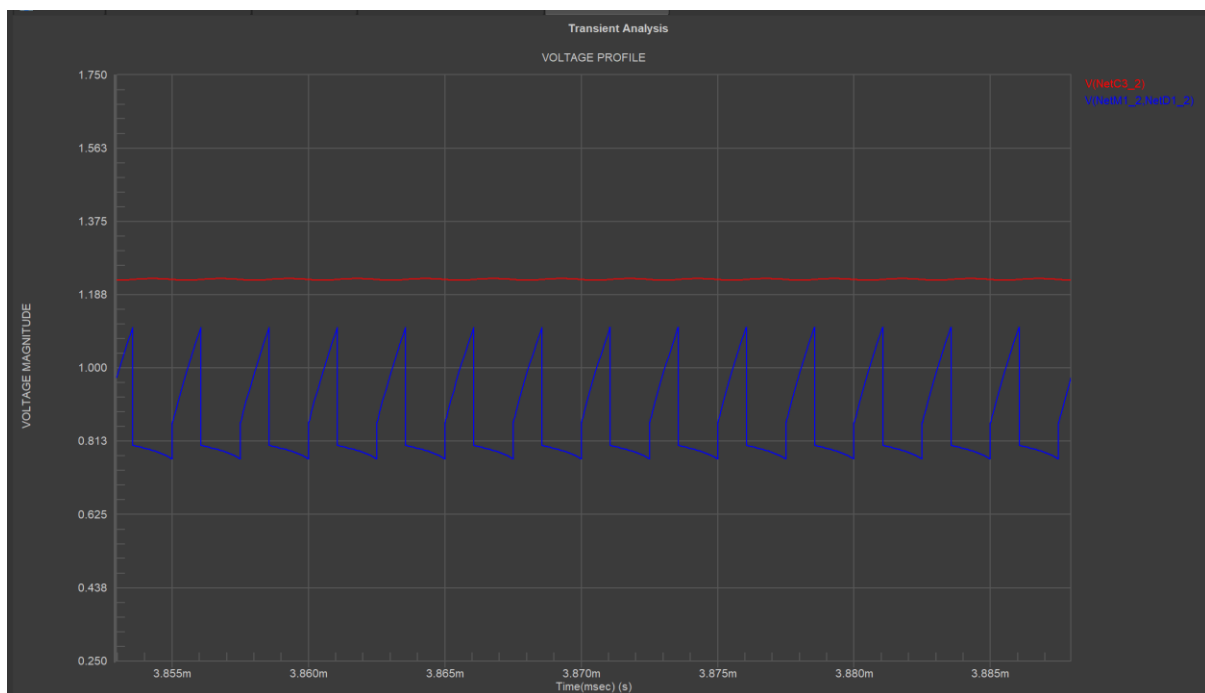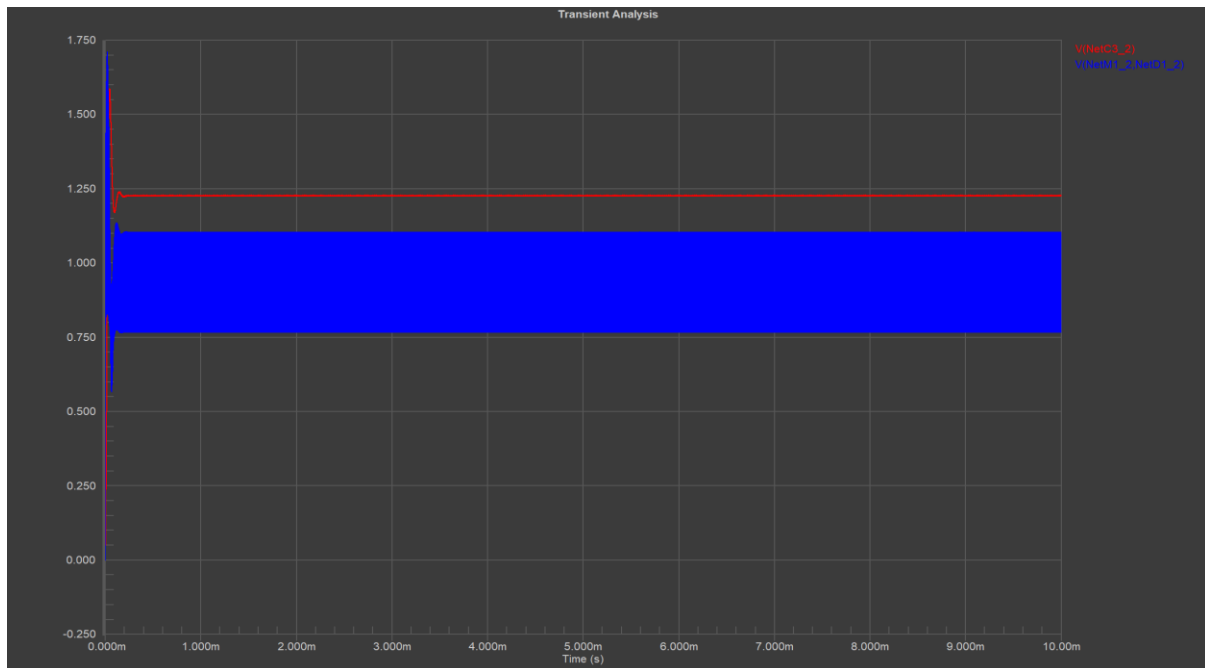


Blue Colour-Voltage across Switch.

Red Colour -Output Voltage.

Drive document: <https://drive.google.com/file/d/1mA1iPQQgpS3Nfb-AqffbJzySsP0CKuUP/view>

➤ **Microcontroller based circuit diagram of buck converter:**


Circuit Diagram of Buck Converter:

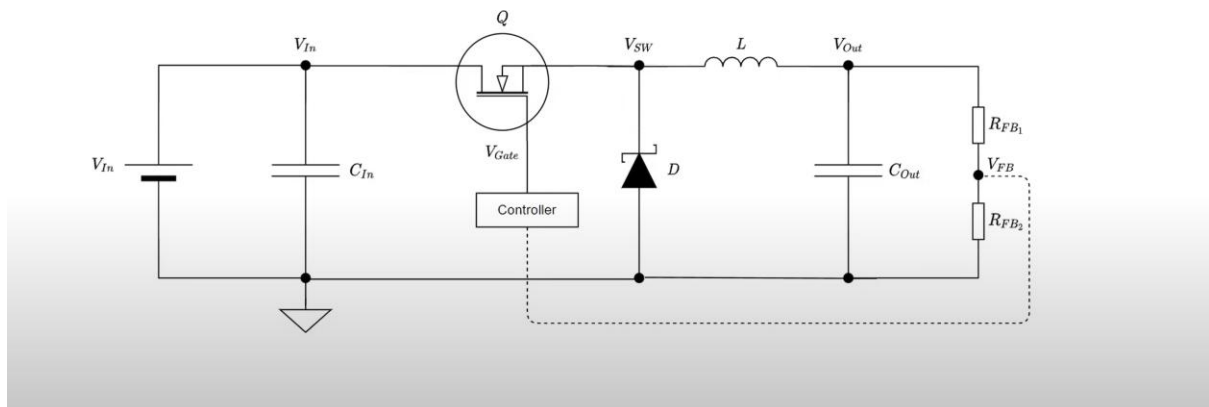


Micro-controlller: STM32F0422G6U6

USB-C Connector: To Supply power i/p and Connect to micro controller.

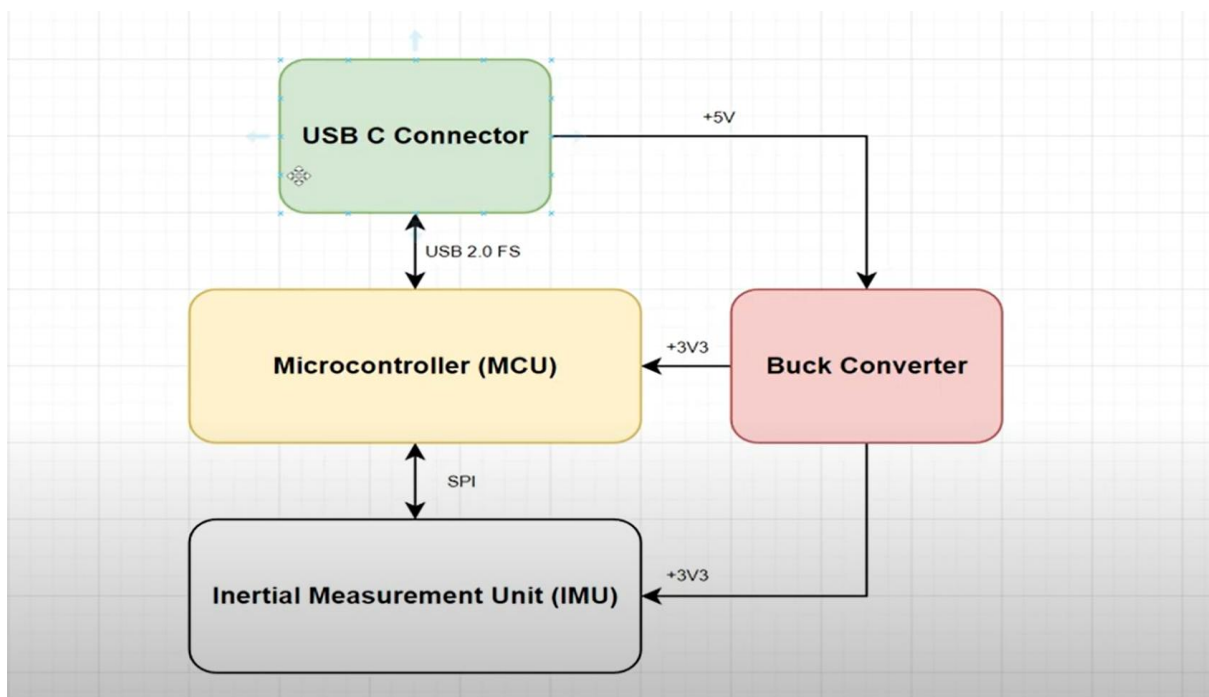Basic block diagram of interconnection of elements:



Microcontroller based Buck Converter:

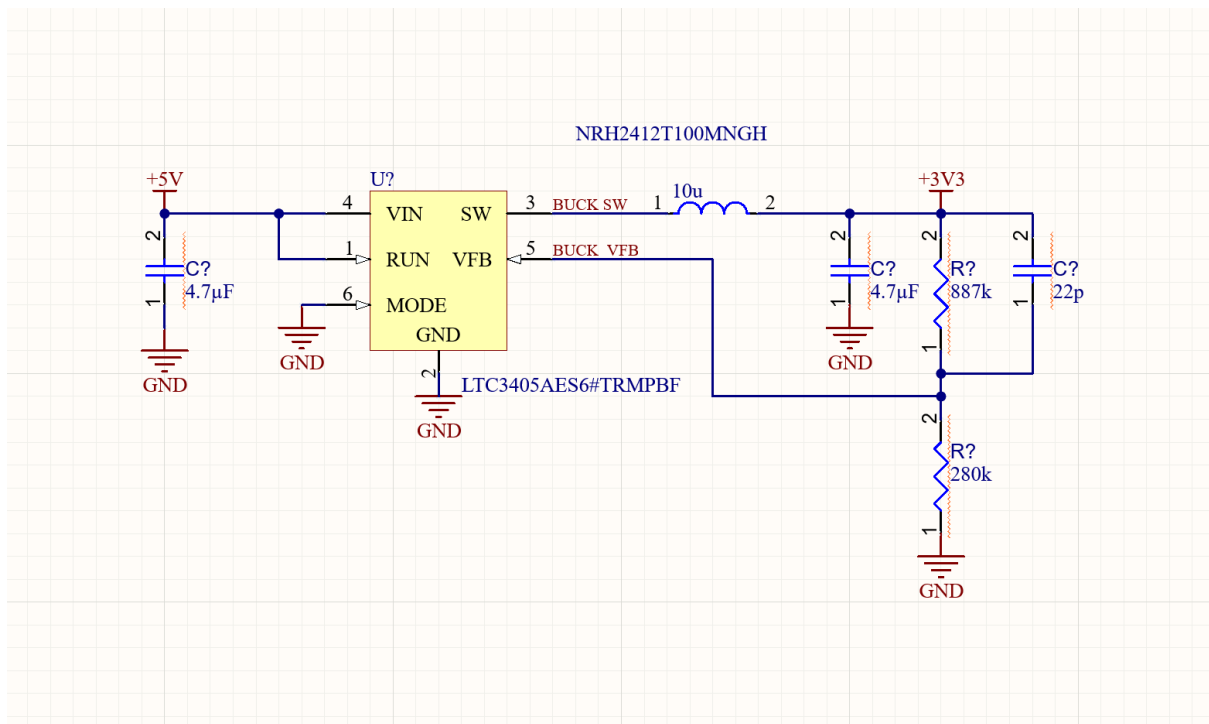

Link for Data Sheet of Microcontroller:

<https://www.st.com/resource/en/datasheet/stm32f042t6.pdf>

Link for Data Sheet of Switching Regulator:

<https://www.analog.com/media/en/technical-documentation/data-sheets/3405afa.pdf>

Link for Data Sheet of Inductor: <https://www.mouser.in/ProductDetail/TAIYO-YUDEN/NRH2412T100MNGH?qs=CNQs48zdnrqx0tE%252BgVC6w%3D%3D&srltid=AfmBOor0vEXebx6fAj6soMOupcZiTu5nCjBRLJ9xWlqlrvjvAjCBzgDu>

Link for Data Sheet of Switching Regulator:

CAPACITOR: CAPC0805(2012)145_L

RESISTOR: RES_0603

Link for Data Sheet of USB_C (USB4105-GF-A):

<https://ww1.microchip.com/downloads/en/appnotes/00001953a.pdf>